

Extra Lab: LTSpice Lab 1

Engineering 100-950

Winter 2020

Learning Objectives

- You will be able to analyze a basic circuit (one without energy storage elements or dependent sources) by hand using Kirchoff's Laws and Nodal Analysis

Learning Assessments

- What is Ohm's Law?
- What are Kirchoff's Voltage Law and Kirchoff's Current Law?
- Do Kirchoff's laws apply to non-ohmic devices?
- Give a brief description of what nodal analysis is
- What are the main steps to performing nodal analysis?

Lab Assignment

Estimated completion time: 0.5 hours +- 30 minutes. Please contact an IA if you are having difficulties and are spending more time than this!

I care more about you trying the problems than the fact that your answers are correct. This is a lot of work and you're not expected to do everything correctly!!

- You will solve a basic problem set of circuit analysis by hand. These problems are designed to be simple and do not have any "tricks" (30-45 minutes).

1 Introduction

In lab, you have explored some basic concepts like voltage and current. Additionally, you have built a voltage divider and explored some interesting circuits.

The goal of this lab is to allow you to explore these concepts further to expose you to some of the basics of Electrical Engineering.

This lab is split into two parts. Here you will build the foundation required to understand what's going on under the hood in LTSpice. In lab 2, you will get to actually play with LTSpice.

Many of the concepts we cover here are a preview of what you might learn in a course like EECS 215. If you enjoy this lab and the concepts of it, please consider taking the course!

If you find these concepts easy, consider completing the advanced version of this lab written by Sarah. In that lab, you get to explore basic first order circuits.

1.1 Credits

All tables and examples are from the EECS 215 course and book. Much of the wording is almost verbatim from the book, though topics were hand picked and distilled to prepare you for this lab. In particular, the course uses 'Circuit Analysis and Design' by Fawwaz T Ulaby, Michael M. Maharbiz, and Cynthia M. Furse.

The assignments are taken directly from Lab 1 of the course, which means that if you choose to take the course, you're already (very slightly) ahead! After this lab you'll have played with LTSpice, which most students entering the course haven't... this will make all the labs significantly easier to work with.

This book can be freely downloaded here. It is not required to complete this lab or understand all the material, but may serve as a helpful reference if you need a more detailed primer than we provide here.

1.2 Disclaimer

This lab glosses over topics I believe were not relevant to being able to complete the end goal of simulation with SPICE (which you will do in lab 2 if you choose to continue). A partial list of some topics that this manual hand-waves over is below, and hopefully if you enjoyed this lab you will go on to explore these in more depth in future classes:

- Dependent voltage and current sources
- Source transforms
- Wye-Delta transforms
- Resistance and conductance at a material level
- Power
- Mesh analysis
- Supernodes

1.3 Pre-requisites

I assume you are familiar with the concepts of charge, current, and voltage. If you are not, please read the ‘Circuits Primer’ on Canvas under [Files](#) [»](#) [Labs](#) [»](#) [Introductory Documents](#) [»](#) [Circuits_Primer.pdf](#).

This is an excellent way to intuitively grasp voltage and how it relates to current.

2 Circuit Basics

2.1 Terminology

Here are some reference tables that will be useful in understanding circuit diagrams. Figure 1 (Table 1-1 from UMF) covers units you might encounter and their symbols, Figure 2 (Table 1-2 from UMF) covers SI units, and Figure 3 (Table 1-3, UMF) shows common circuit elements.

Table 1-1: Fundamental and electrical SI units.

Dimension	Unit	Symbol
Fundamental:		
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric charge	coulomb	C
Temperature	kelvin	K
Amount of substance	mole	mol
Luminous intensity	candela	cd
Electrical:		
Current	ampere	A
Voltage	volt	V
Resistance	ohm	Ω
Capacitance	farad	F
Inductance	henry	H
Power	watt	W
Frequency	hertz	Hz

Figure 1: SI Units and Symbols

Some important terms we will formalize:

- Node: An electrical connection point that connects multiple circuit elements
 - Note that we often draw things in a way that’s easy to visualize, but really anything connected by the same wire with no circuit elements in between is part of the same node.

Table 1-2: Multiple and submultiple prefixes.

Prefix	Symbol	Magnitude
exa	E	10^{18}
peta	P	10^{15}
tera	T	10^{12}
giga	G	10^9
mega	M	10^6
kilo	k	10^3
milli	m	10^{-3}
micro	μ	10^{-6}
nano	n	10^{-9}
pico	p	10^{-12}
femto	f	10^{-15}
atto	a	10^{-18}

Figure 2: SI Prefixes

- Branch: Trace between two consecutive nodes with only one element in between them
- Loop: Closed path with the same start and end node
- Mesh: A restricted kind of loop: it is a loop that encloses no other loops
- In series: elements that share the same current
- In parallel: elements that share the same voltage

2.2 Reference nodes

One thing many of you struggled with during labs was understanding the importance of ground.

The big idea is that voltage is by definition between two points. However, for convenience sometimes we like to assign a particular node to be our ground node, so that we can measure all our voltages relative to this.

Say we have a circuit and we are measuring the voltage between two nodes, a and b. Then $V_{ab} = V_a - V_b$. Now let's say that we make all future measurements relative to node b... let us assign node b to be our reference point by calling it ground. Now we are allowed to simply refer to V_a and it is implied that it is relative to ground (node b).

2.3 The Resistor

A resistor is a device which impedes current. It always drops voltage.

A resistor is an excellent example of an almost perfect "Ohmic" device. An ohmic device is one which follows Ohm's Law, $V = IR$, at least for some particular range of current (called the linear region).

Table 1-3: Symbols for common circuit elements.


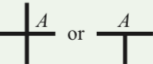





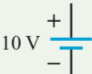



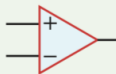

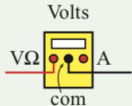
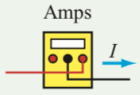



		
Conductor (wire)	Two conductors electrically joined at node A	Two conductors not joined electrically
		
Fixed-value resistor	Variable resistor	Capacitor
		
Inductor	10 V dc battery	12 V ac source
		
6 A current source	Switch	Operational amplifier
		
Transistor	Volts V Ω A com Voltmeter	Amps Ammeter
		
Dependent voltage source	Dependent current source	Light-emitting diode (LED)

Figure 3: Common Circuit Elements

Not all devices follow this relationship! Elements like diodes are nonlinear and we cannot use Ohm's law for these.

2.4 Passive Sign Convention

There are two ways to assign polarity to an element with current entering it.

We will choose to assign current entering a device to be defined as entering the (+) side of v . We will not cover power in this lab, but this effectively means that any circuit elements dissipating power will have a $P > 0$, and any elements supplying power will have a $P < 0$.

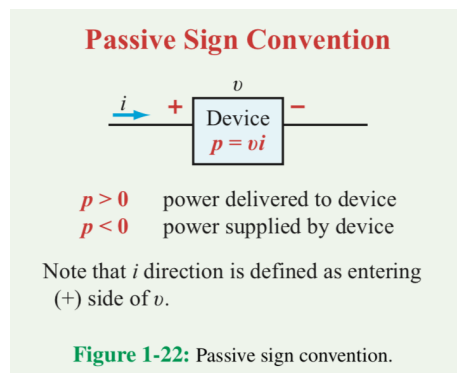


Figure 4: Passive Sign Convention

3 Circuit Analysis Fundamentals

All circuit theory is built on a pretty small set of fundamental laws, of which KCL and KVL are the most important.

The most interesting thing is that these laws are ALWAYS true; they are built upon fundamental laws of conservation of energy. This means that even if you have a non-ohmic device, you absolutely can still write these equations and they will hold.

3.1 Kirchoff's Current Law (KCL)

In an ideal circuit, a node is unable to store, generate, or dissipate electric charge. Thus, all current entering a node must equal all current leaving a node.

In other words, the sum of all currents entering a node must equal 0.

Here is a good video on KCL.

3.2 Kirchoff's Voltage Law (KVL)

The law of conservation of energy states that if electric charge is moved around a closed loop (where end position = start position), then the net gain or loss of energy must be 0.

Voltage is related to potential energy, thus the algebraic sum of voltages around a closed loop must be 0.

In terms of getting the signs right, follow these two rules and you'll get the right equation every time:

1. Go around your loop in a clockwise fashion
2. Assign a positive sign to your KVL equation if you encounter the (+) side of an element first, and a negative sign if you encounter the (-) side first

If you would like a video on KVL, here is our recommendation.

<https://www.khanacademy.org/science/electrical-engineering/ee-circuit-analysis-topic/ee-dc-circuit-analysis/v/ee-labeling-voltages>.

3.3 Application of Fundamental Laws 1

Using KVL, KCL and Ohm's Law solve for all unknown currents and voltages in the circuit in Figure 5.

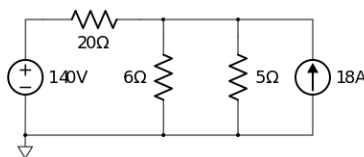


Figure 5: Circuit for Application of Fundamental Laws 1

3.4 Bonus Problem: Application of Fundamental Laws 2

This problem is not required for completion of this lab because it contains two voltage sources. You should still give it a try if you have time!

Using KVL, KCL, and Ohm's Law, solve for v_1 , v_2 , v_3 , i_1 , i_2 , and i_3 in the circuit in Figure 6.

3.5 Nodal Analysis

It would be nice to have a codified set of steps to solve for all voltages and currents in a circuit.

If you have taken physics in high school or Physics 240, you know that it can be frustrating to throw KVL/KCL mindlessly at a circuit and hope to get a set of linearly independent equations to solve the circuit problem at hand.

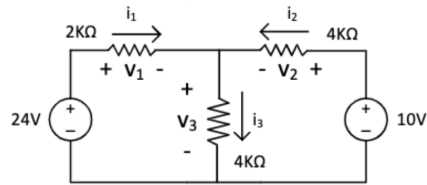


Figure 6: Circuit for Bonus Problem

The Node Voltage Method is an organized and efficient way of approaching any circuit and is based off of Kirchhoff's Current Law.


The goal of the method we present is a way to mindlessly solve a circuit.

Steps for Nodal Analysis:

1. Identify all nodes in the circuit
2. Choose a ground node
3. Generate a KCL equation for each non-reference node. An easy way to make this mindless is to always form the sum of currents leaving the node (assigning a negative sign to any current entering the node).
4. Generate a KVL expression for each voltage source representing the drop between 2 nodes connected by the voltage source
5. Solve the independent simultaneous equations using a solver program like MATLAB.

Please watch this video for a good overview of the process. The video uses a slightly different set of steps that perform the same analysis.

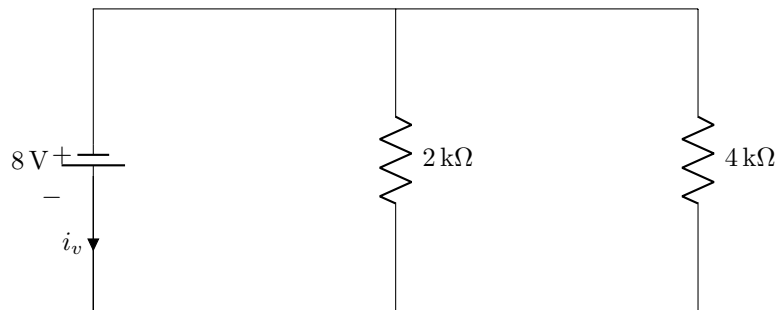3.6 Example of Nodal Analysis: Battery with Two Parallel Resistors




Let us perform the steps listed:

1. There are 2 nodes in this circuit (above and below the battery).

- Note that even though there are 3 branches, all the top wires of the branches connect into a common wire with no circuit elements between them, thus they are part of the same node (the positive terminal of our battery). Similarly, all the bottom wires of the branches connect into one wire and form the second node (the negative terminal of the battery).
 - Let's call the bottom node V_0 and the top node V_1 .
- Let's just choose the bottom node to be ground (thus the negative terminal of the battery is at 0V).
 - There is one non reference node. Let's write KCL for it!
 - $i_v + \frac{V_1}{2\text{k}\Omega} + \frac{V_1}{4\text{k}\Omega} = 0$
 - Let's generate a KVL expression for our one voltage source.
 - $V_1 - 0\text{V} = 8\text{V}$
 - We can now solve for V_1 and i_v ! Plugging in and solving our system yields $V_1 = 8\text{V}$ (somewhat obviously) and $i_v = 6\text{A}$

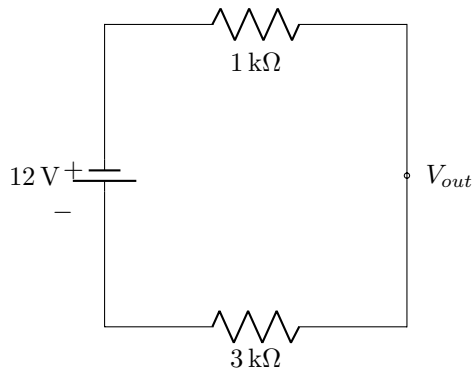3.7 Example of Nodal Analysis: Voltage Divider



You have already explored voltage dividers in lab! To refresh your memory, here is the formula for a voltage divider with 2 resistors: $V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$.

Using this formula, we can see from the diagram that we expect $V_{out} = \frac{3}{4} * 12\text{V} = 9\text{V}$.

Let's use nodal analysis to verify this result! Note that by not labeling "obvious" nodes (like ones with only a battery separating them from ground), we can sometimes reduce the number of equations we need to write.

- There are 3 nodes in this circuit: on either side of the battery, and V_{out}
- Let's choose the bottom terminal of the battery to be ground. The node at the positive terminal of the battery is clearly 12 Volts then, so we won't bother labeling it, since it's already solved.

3. There is only one unsolved non-reference node: V_{out} . Let's write a KCL expression for it!

•

$$\frac{V_{out} - 12 \text{ V}}{1 \text{ k}\Omega} + \frac{V_{out} - 0 \text{ V}}{3 \text{ k}\Omega} = 0$$

4. Since we didn't bother to label the node above the voltage source and just directly solved for it, we do not need to write a KVL expression for the voltage source.
5. We can now solve for V_{out} to obtain that $V_{out} = 9 \text{ V}$, just as expected!

3.8 Application of Nodal Analysis

Apply nodal analysis to determine the current I in Figure 7. There are many ways to do this. If you are struggling, watch the video linked before the assignments! You can use MATLAB to solve the equations if needed, though it should be trivial to do by hand.

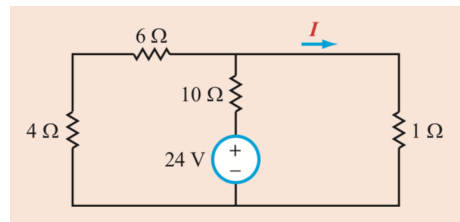


Figure 7: Circuit schematic for assignment on nodal analysis

What to submit for this lab

1. Your solution to "Application of Fundamental Laws 1"
 - Include all equations and any diagrams you drew to solve this problem (if any)
2. Your solution to "Application of Nodal Analysis"
 - Include all equations and any diagrams you drew to solve this problem (if any)
3. Don't forget to Slack message either Neil or Sarah!